

**Applications:**

Medium current range - 0 to 8 amps. Peak Current 22 amps < 1sec. High stray field immunity and high sensitivity

**Operation:**

Output voltage can be measured between A1OUT and A2OUT for a differential output. The output voltage can be as high as +/- 5volts because of the differential output. Current in the direction shown, will produce a positive going output. Current in the opposite direction will produce a negative going output. AC current will produce an AC analog output. The output sensitivity level is approximately 210 mV/amp. Because the two IC's see the same external fields, the resulting differential voltage is canceled out. Supply voltage, VDD, and outputs are protected with 6.2 volt zeners.

